

A boy and girl have been investigating circuits using three bulbs and three cells. The results are shown:

Series			Series	
1	*		1	***
2	**		2	**
3	***		3	*
Series			Parallel	
1	0.16		1	0.16
2	0.16		2	0.32
3	0.17		3	0.47
Parallel			Parallel	
1	**		1	0.6
2	**		2	0.3
3	**		3	0.3

There is a slight problem though! The pair coloured in each heading and wrote in the circuit they used but forgot to write what each heading is! ☹

Study the tables closely.

1. Write down the correct heading for each table and present your answer in a table
2. Choose any one of these result tables and complete a report. The evaluation should attempt to explain the results in the table.